



# Masoud Heidary

think outside the box

CA Lab – EX4

برای ساخت even parity generator میدانیم با xor کردن ورودی ها میتوانیم خروجی parity bit را برای ساخت بدست آوریم.



به این صورت کد را به صورت زیر داریم

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity ParityGenerator is
   Port ( Data : in STD_LOGIC_VECTOR (7 downto 0);
           En : in STD_LOGIC;
           P : out STD_LOGIC);
end ParityGenerator;
architecture Behavioral of ParityGenerator is
process(Data, En)
   if En = '1' then
        P <= Data(0) xor Data(1) xor Data(2) xor Data(3) xor
            Data(4) xor Data(5) xor Data(6) xor Data(7);
   end if;
end process;
end Behavioral;
```

### test bench:

```
-- Stimulus process
stim_proc: process
begin


Data <= "000000000";
En <= '0';
wait for 10 ns;


En <= '1';
wait for 10 ns;

Data <= "00000001";
wait for 10 ns;

wait;
end process;
```

### output:

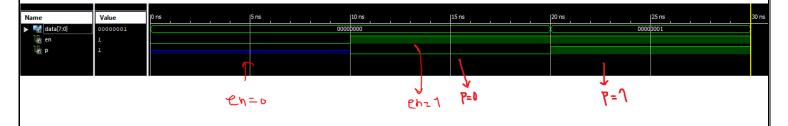

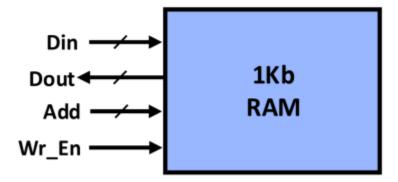

memory به سايز 1kbit، در واقع 128-byte است، که به 7 خط آدرس نياز دارد

```
type RAM_128B is array (0 to 127) of STD_LOGIC_VECTOR (7 downto 0);
    signal RAM: RAM_128B := (others => (others => '0'));
```

و کد نویسی به صورت زیر میشود

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;
entity Memory128Byte is
   Port ( Din : in STD_LOGIC_VECTOR (7 downto 0);
           Dout : out STD_LOGIC_VECTOR (7 downto 0);
           Address: in STD_LOGIC_VECTOR (6 downto 0);
           RW : in STD_LOGIC);
end Memory128Byte;
architecture Behavioral of Memory128Byte is
   type RAM_128B is array (0 to 127) of STD_LOGIC_VECTOR (7 downto 0);
    signal RAM: RAM_128B := (others => '0'));
process (Din, Address, RW)
   if RW = '0' then
        Dout <= RAM(to_integer(unsigned(Address)));</pre>
   elsif RW = '1' then
        RAM(to_integer(unsigned(Address))) <= Din;</pre>
end process;
end Behavioral;
```

### test bench:

```
-- Stimulus process

stim_proc: process

begin
    wait for 10 ns;

Address <= "00000001";
    RW <= '0';
    wait for 10 ns;

Din <= "11110000";
    RW <= '1';
    wait for 10 ns;

Din <= "000000000";
    RW <= '0';
    wait for 10 ns;

wait;
end process;
```

## output:

