



Masoud Heidary

think outside the box

CA Lab – EX6

MasoudHeidaryMH@gmail.com

## شمارنده BCD

برای طراحی این شماره از machine state استفاده کرده و با آمدن هر کلاک بالارونده به حالت بعدی میرویم، واضح است با هر تغییر حالت خروجی را نیز باید آبدیت نماییم.

برای پایه ریست نیز، به این صورت عمل میکنیم که هر زمانی فعال شد حالت مدار به صفر تغییر میدهیم و تا زمانی که ریست فعال است از تغییر حالت مدار جلوگیری میکنیم.

Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity FSM_BCD is
    Port ( clk : in  STD_LOGIC;
          reset : in  STD_LOGIC;
          output : out  STD_LOGIC_VECTOR (3 downto 0));
end FSM_BCD;

architecture Behavioral of FSM_BCD is
    type state_type is (D0, D1, D2, D3, D4, D5, D6, D7, D8, D9);
    signal state: state_type := D0;
begin

    -- STATE process
    process (clk, reset)
    begin
        -- reset pin config
        if reset = '1' then
            state <= D0;

            -- change state by clk
        elsif rising_edge(clk) then
            case state is
                when D0 =>
                    state <= D1;
                when D1 =>
                    state <= D2;
                when D2 =>
                    state <= D3;
```

```

        when D3 =>
            state <= D4;
        when D4 =>
            state <= D5;
        when D5 =>
            state <= D6;
        when D6 =>
            state <= D7;
        when D7 =>
            state <= D8;
        when D8 =>
            state <= D9;
        when D9 =>
            state <= D0;
        end case;
    end if;
end process;

-- change output based on state
process (state)
begin
    case state is
        when D0 =>
            output <= "0000";
        when D1 =>
            output <= "0001";
        when D2 =>
            output <= "0010";
        when D3 =>
            output <= "0011";
        when D4 =>
            output <= "0100";
        when D5 =>
            output <= "0101";
        when D6 =>
            output <= "0110";
        when D7 =>
            output <= "0111";
        when D8 =>
            output <= "1000";
        when D9 =>
            output <= "1001";
        end case;
    end process;

```

```
end Behavioral;
```

نوع پیاده سازی شده machine state نیز از یکی از مطالب شرکت اینتل ایده گرفته شده است


[link](#)

(if link didn't work)


[https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/hdl/vhdl/vhdl\\_pro\\_state\\_machines.htm#:~:text=A%20state%20machine%20is%20a,and%20the%20next%2Dstate%20logic](https://www.intel.com/content/www/us/en/programmable/quartushelp/13.0/mergedProjects/hdl/vhdl/vhdl_pro_state_machines.htm#:~:text=A%20state%20machine%20is%20a,and%20the%20next%2Dstate%20logic).

Test Bench:

Reset Pin

 


Counting

 
 
## مولد سیگنال

اگر سیگنال خروجی را به صورت state های مختلفی از یک state machine بدانیم، میتوانیم سیگنال را به صورت زیر تجسم کنیم



حال میتوانیم مانند مثال قبلی، با آمدن کلاک تنها به state بعدی برویم و خروجی را نیز update کنیم.

### Code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity FSM_Signal is
    Port ( clk : in  STD_LOGIC;
          output : out  STD_LOGIC);
end FSM_Signal;

architecture Behavioral of FSM_Signal is
    type state_type is (S0, S1, S2, S3, S4);
    signal state: state_type := S4;
begin

    process (clk)
    begin
        if rising_edge(clk) then
            case state is
```

```

        when S0 =>
            state <= S1;
        when S1 =>
            state <= S2;
        when S2 =>
            state <= S3;
        when S3 =>
            state <= S4;
        when S4 =>
            state <= S0;
    end case;
end if;
end process;

-- change output based on state
process (state)
begin
    case state is
        when S0 =>
            output <= '1';
        when S1 =>
            output <= '0';
        when S2 =>
            output <= '1';
        when S3 =>
            output <= '0';
        when S4 =>
            output <= '0';
    end case;
end process;
end Behavioral;

```

Test Bench:

