

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_UNSIGNED.ALL;
4 use IEEE.NUMERIC_STD.ALL;
5
6
7 entity ALU is
8     Port ( A : in      STD_LOGIC_VECTOR (7 downto 0);
9           B : in      STD_LOGIC_VECTOR (7 downto 0);
10          F : out      STD_LOGIC_VECTOR (7 downto 0);
11          Cin : in     STD_LOGIC;
12          OPCODE : in  STD_LOGIC_VECTOR (3 downto 0);
13          Cout : out   STD_LOGIC);
14 end ALU;
15
16 architecture Behavioral of ALU is
17
18     -- signals
19     signal A_add_Cin:   STD_LOGIC_VECTOR (7 downto 0);
20     signal A_add_B:     STD_LOGIC_VECTOR (7 downto 0);
21     signal Sub:         STD_LOGIC_VECTOR (7 downto 0);
22     signal R_SHIFT:     STD_LOGIC_VECTOR (7 downto 0);
23     signal L_SHIFT:     STD_LOGIC_VECTOR (7 downto 0);
24
25     signal Carry:       STD_LOGIC_VECTOR (2 downto 0);
26
27     COMPONENT ADD8
28     PORT(
29         A : IN          std_logic_vector(7 downto 0);
30         B : IN          std_logic_vector(7 downto 0);
31         Cin : IN        std_logic;
32         Sum : OUT       std_logic_vector(7 downto 0);
33         Cout : OUT      std_logic
34     );
35 END COMPONENT;
36 begin
37
38     -- A + Cin
39     Inst_ADD8_0: ADD8 PORT MAP(
40         A => A,
41         B => "00000000",
42         Cin => Cin,
43         Sum => A_add_Cin,
```

```
44     Cout => Carry(0)
45 );
46
47 -- A + B + Cin
48 Inst_ADD8_1: ADD8 PORT MAP(
49     A => A,
50     B => B,
51     Cin => Cin,
52     Sum => A_add_B,
53     Cout => Carry(1)
54 );
55
56 -- A + (not B) + Cin
57 Inst_ADD8_2: ADD8 PORT MAP(
58     A => A,
59     B => (not B),
60     Cin => Cin,
61     Sum => Sub,
62     Cout => Carry(2)
63 );
64
65 -- shift to right
66 R: for i in 0 to 6 generate
67     R_SHIFT(i) <= A(i+1);
68 end generate;
69 R_SHIFT(7) <= '0';
70
71 -- shift to left
72 L: for i in 1 to 7 generate
73     L_SHIFT(i) <= A(i-1);
74 end generate;
75 L_SHIFT(0) <= '0';
76
77
78 with OPCODE (3 downto 0) select
79     F <=  A_add_Cin  when "0000",
80           A_add_B    when "0001",
81           Sub        when "0010",
82           A-1        when "0011",
83           A and B     when "0100",
84           A or B      when "0101",
85           A xor B     when "0110",
86           not A       when "0111",
```

```
87         R_SHIFT      when "1000",
88         R_SHIFT      when "1001",
89         R_SHIFT      when "1010",
90         R_SHIFT      when "1011",
91         L_SHIFT      when "1100",
92         L_SHIFT      when "1101",
93         L_SHIFT      when "1110",
94         L_SHIFT      when "1111",
95         "ZZZZZZZZ"  when others;
96
97     with OPCODE (3 downto 0) select
98         Cout <= Carry(0) when "0000",
99         Carry(1) when "0001",
100        Carry(2) when "0010",
101        '0'      when others;
102
103 end Behavioral;
```